

4.16 A four-port network has the scattering matrix shown below.

- (a) Is this network lossless?
- (b) Is this network reciprocal?
- (c) What is the return loss at port 1 when all other ports are terminated with matched loads?
- (d) What is the insertion loss and phase delay between ports 2 and 4, when all other ports are terminated with matched loads?

- (e) What is the reflection coefficient seen at port 1 if a short circuit is placed at the terminal plane of port 3, and all other ports are terminated with matched loads?

$$[S] = \begin{bmatrix} 0.1 \angle 90^\circ & 0.8 \angle -45^\circ & 0.3 \angle -45^\circ & 0 \\ 0.8 \angle -45^\circ & 0 & 0 & 0.4 \angle 45^\circ \\ 0.3 \angle -45^\circ & 0 & 0 & 0.6 \angle -45^\circ \\ 0 & 0.4 \angle 45^\circ & 0.6 \angle -45^\circ & 0 \end{bmatrix}.$$